

# DDR System Design Considerations

**Integrated Technology Group  
Micron**




# DDR Overview




# SSTL2 Signal Levels


Driver

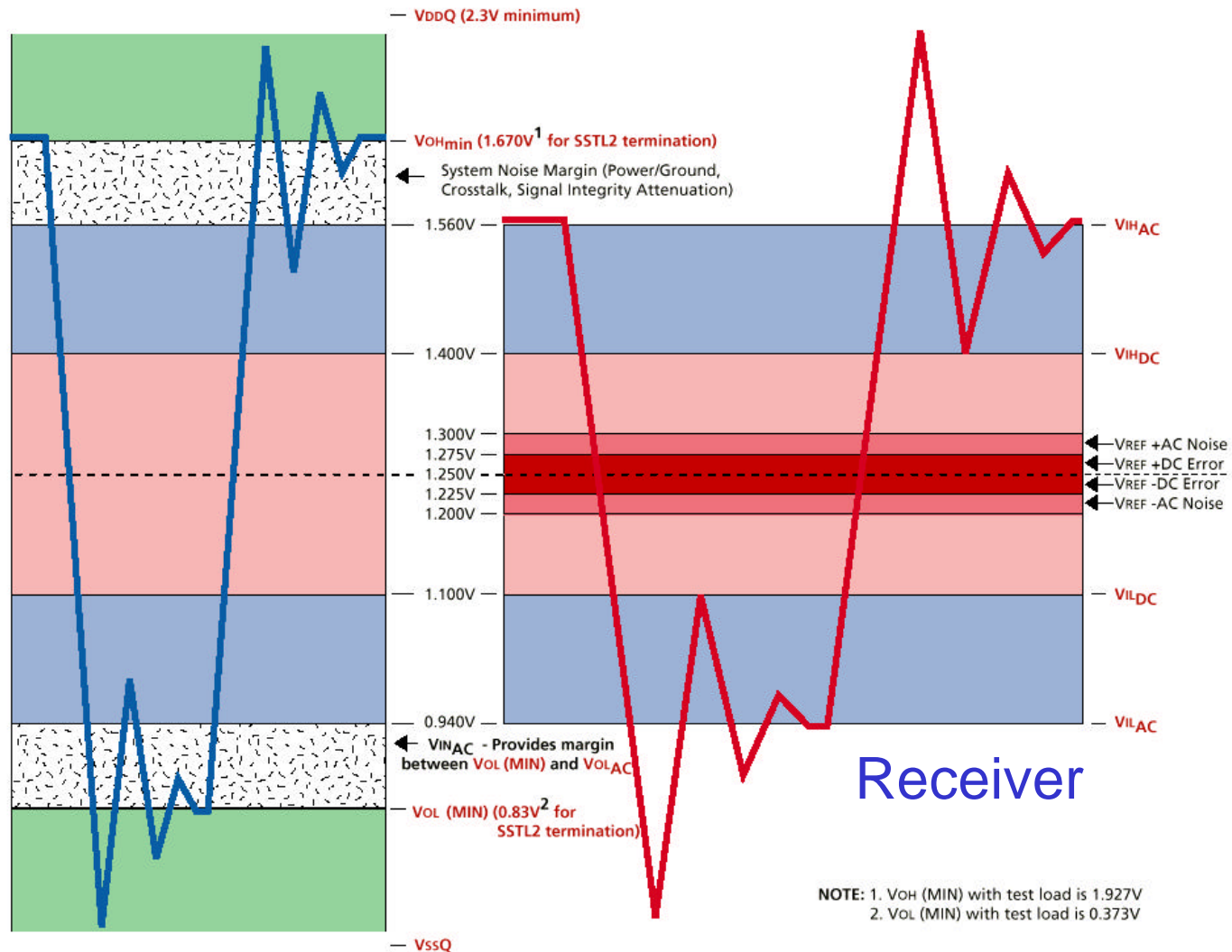

# SSTL2 Double Ended Termination

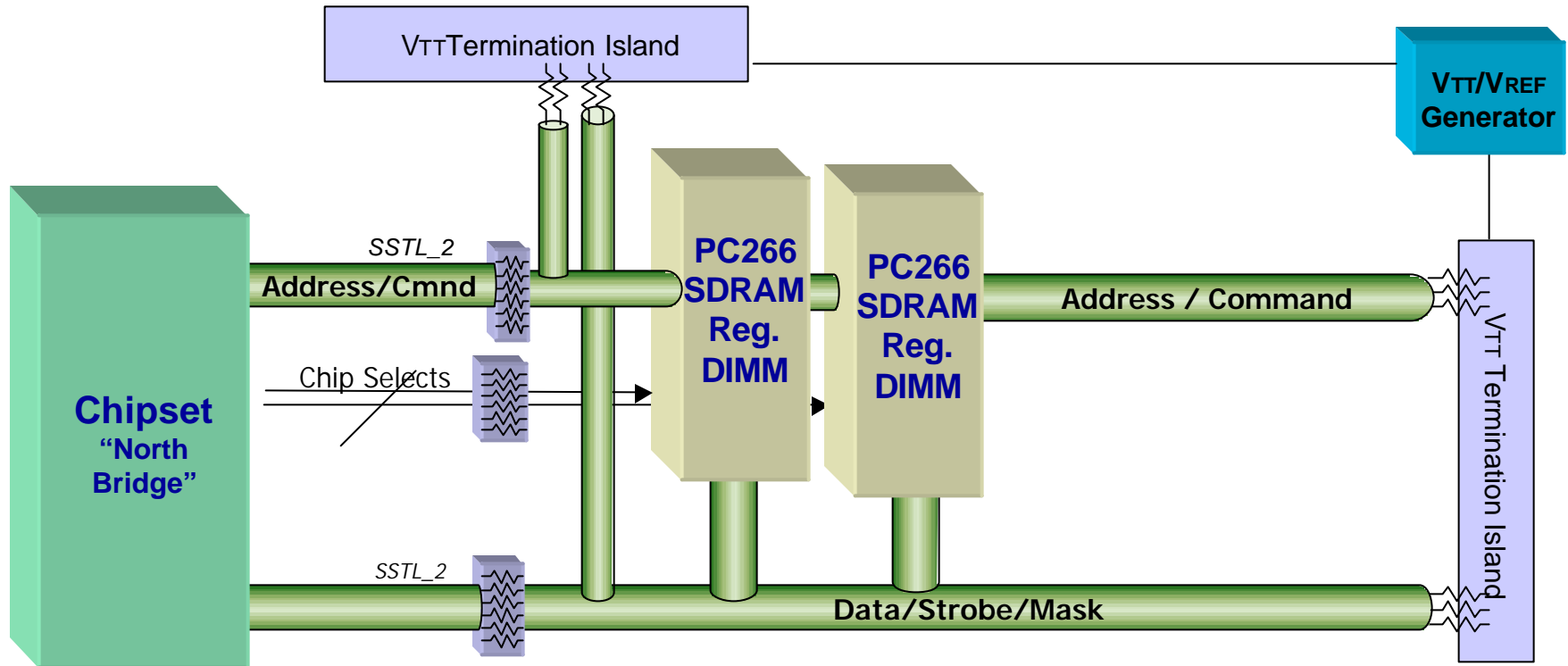

# SSTL2 Single Ended Termination

 


# Use Single Parallel Termination Resistor With Series Resistor

- Lower system cost
- Easier motherboard route
- Improved bandwidth
- Lower skew due to ISI
- Reduced skew due to crosstalk if done properly
  - Consider crosstalk effects in the connector pinout



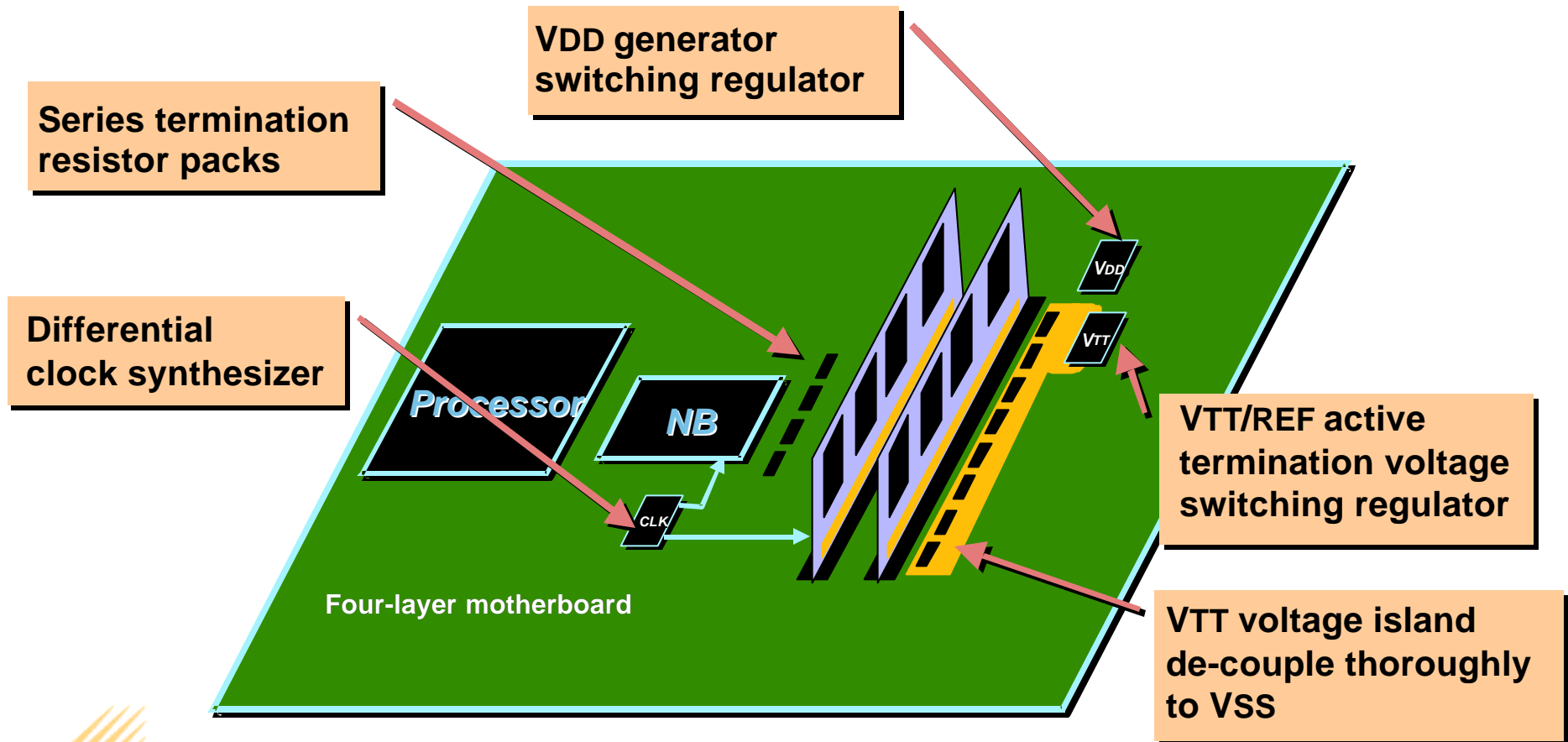
# Double Data Rate Motherboard Components


 
# Typical Signaling for DDR Main Memory

- The values for the series and termination resistors vary depending on the system design





# VTT/VREF Implementation





# Goals of VTT and VREF Design

- **Minimize timing skew due to**
  - Asymmetric logic highs versus logic lows
  - Noise on VREF or VTT
  - Offset of VTT relative to VREF
  - Drift of VREF or VTT over voltage and temperature
  - External component mismatch
- **Minimize cost**
- **Minimize power dissipation**

# VREF Requirements

- **Track 50% of ( $V_{DDQ}$ - $V_{SSQ}$ ) over**
  - Voltage
  - Temperature
  - Noise
- **Supplies minimal DC current (input leakage only) and only small transient currents**
  - Input to NFET gates of a differential pair

# VREF Tracking to VDDQ

 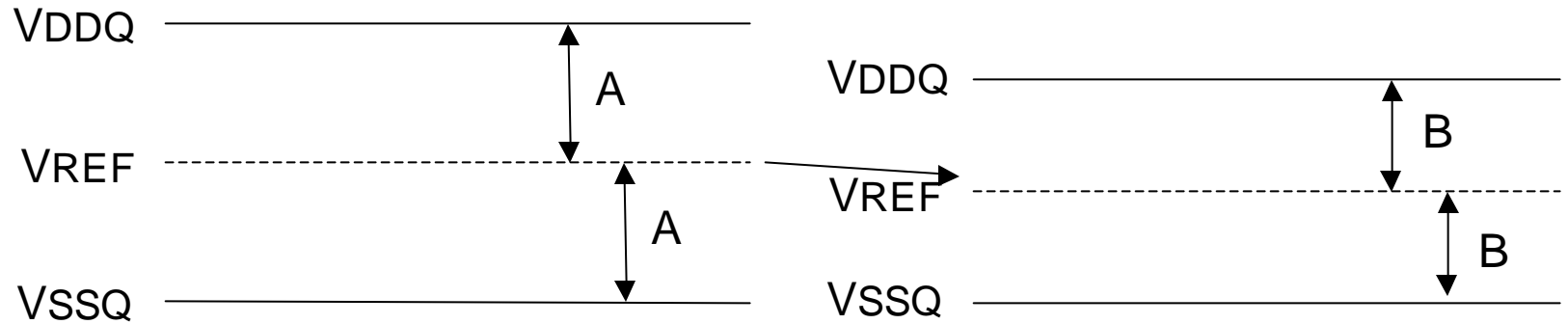


# VREF Recommendations

- **Use global VREF distribution scheme**
  - Eliminates variation and tracking of multiple generators
  - Best performance if kept clean
- **Use simple resistor divider with 1% or better accuracy**
  - Inexpensive to use
  - Tracks voltage and temperature well
- **Use VREFOUT pin of ML6554**
  - Resistor divider is integrated on-chip
  - Fewer external components
  - Best accuracy and matching to VTT due to trimming
  - Minimizes DC error caused by the load current of multiple device input leakage



# VREF Generation

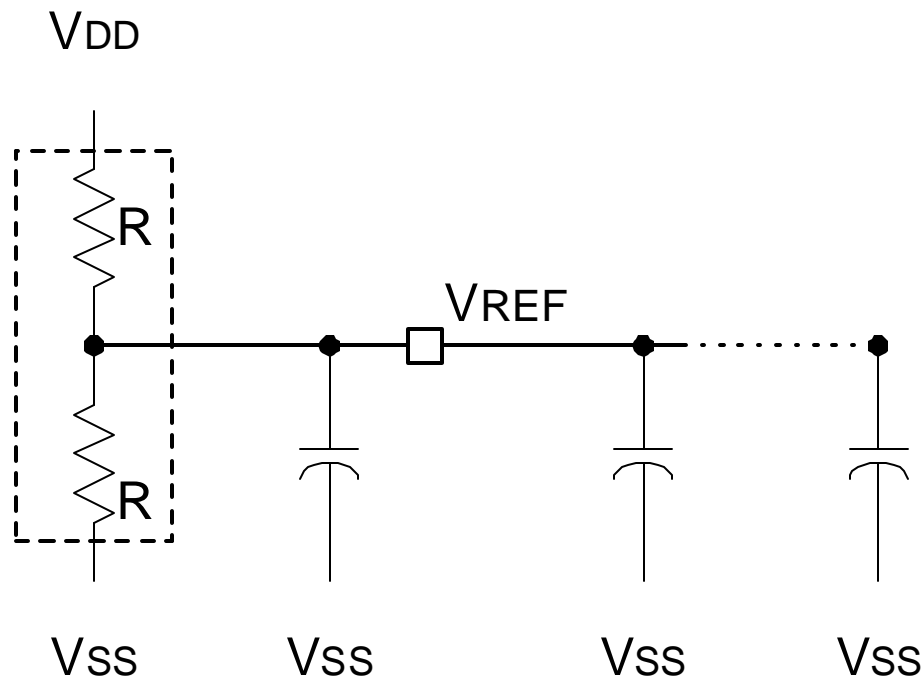- Example of VREF generation using a resistor divider




Discrete Resistors or VREF (OUT) of ML6654

# VREF Layout Recommendations

- **Maintain a 15-20 mil clearance from other nets**
- **Use distributed decoupling scheme**
  - **Minimizes capacitor ESL**
  - **Localizes transient currents and returns**
- **Simple implementation by routing on top signal layer trace**
  - **VREF is at connector pin 1**
  - **Isolate VREF and/or shield with VDDQ and VSSQ**

# VREF PCB Routing

 



# VTT Requirements

- **Track 50% of ( $V_{DDQ}$ - $V_{SSQ}$ ) over**
  - Voltage
  - Temperature
  - Noise
- **Maintain  $<40\text{mV}$  offset from  $V_{REF}$  over these conditions**
- **Source and sink DC current for signal termination**
  - Absolute maximum current is 2.6-2.9A for a 64/72-bit channel

# VTT Recommendations

- **Several solutions exist that are tradeoffs of cost, integration, and performance**
  - **Standard analog components (Motorola, National, Fairchild, etc.)**
    - **High current output, good accuracy**
  - **Switching regulator with discrete MOSFETs (such as LTC1430)**
    - **High current output (10A), good accuracy, semi-integrated**
  - **Switching regulator with integrated MOSFETs (such as ML6554)**
    - **Adequate current output (3A) and accuracy, highest integration, lowest cost**

# VTT Recommendations

## (continued)

- **Use global  $V_{REF}$  as input reference to minimize tracking error and offset**
- **Use high-quality filter components**
  - **Low  $R_s$  on filter inductor**
  - **Low ESR and ESL on filter capacitor to minimize DC and dynamic offset**
    - **Recommend the use of multiple parallel capacitors and/or Sanyo OS-CONs to minimize ESR and ESL**



# VTT Layout Recommendations

## ○ Decouple to Vssq


- Decouple at both ends, and distribute decoupling across the island to localize transient currents and minimize ESL

## ○ Place termination resistors on a top layer VTT island

- Island is at the end of the bus and non-obstructing
- Use wide-island trace for current capacity
- Place VTT generator as close to termination resistors as possible to minimize impedance (inductance)




# VTT Island PCB Layout

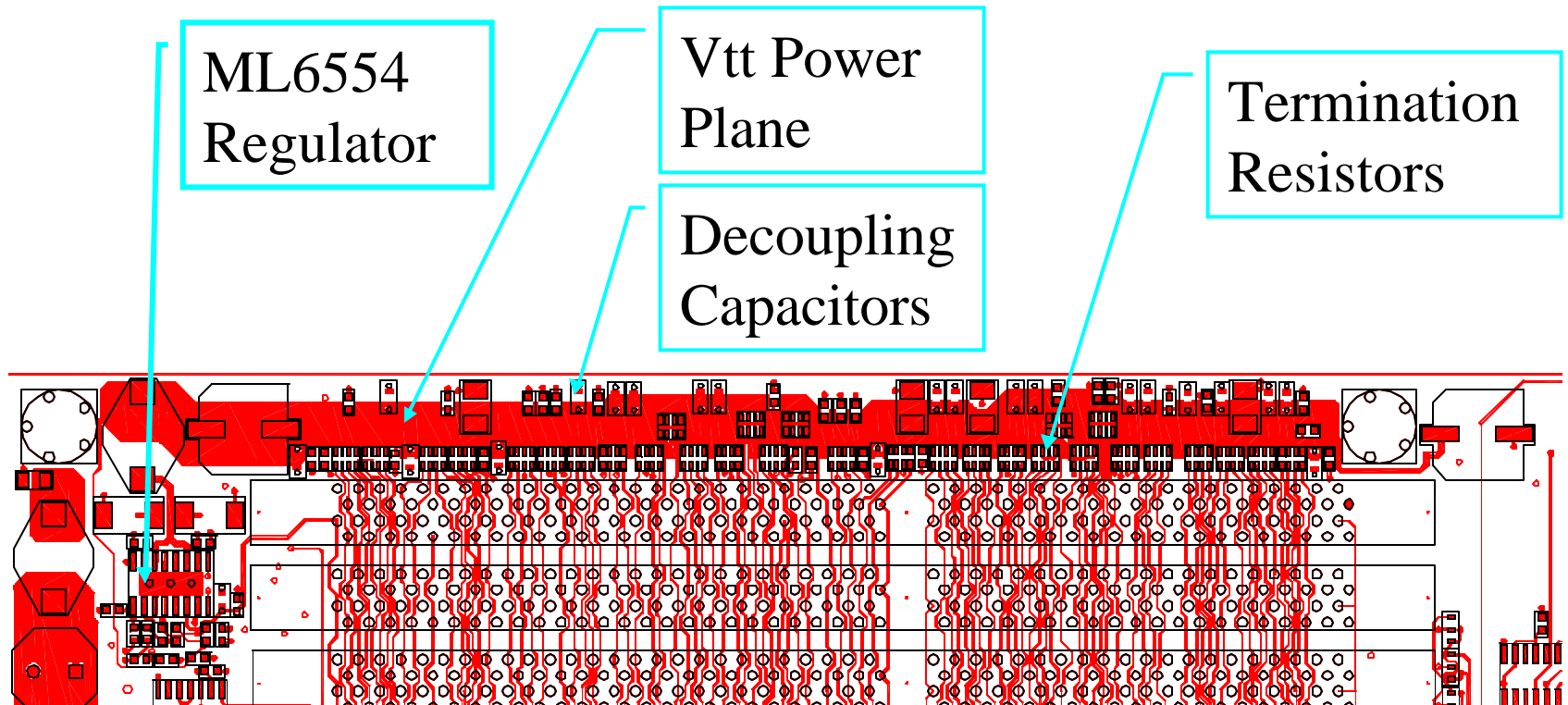


# 2.5 Volt Regulation

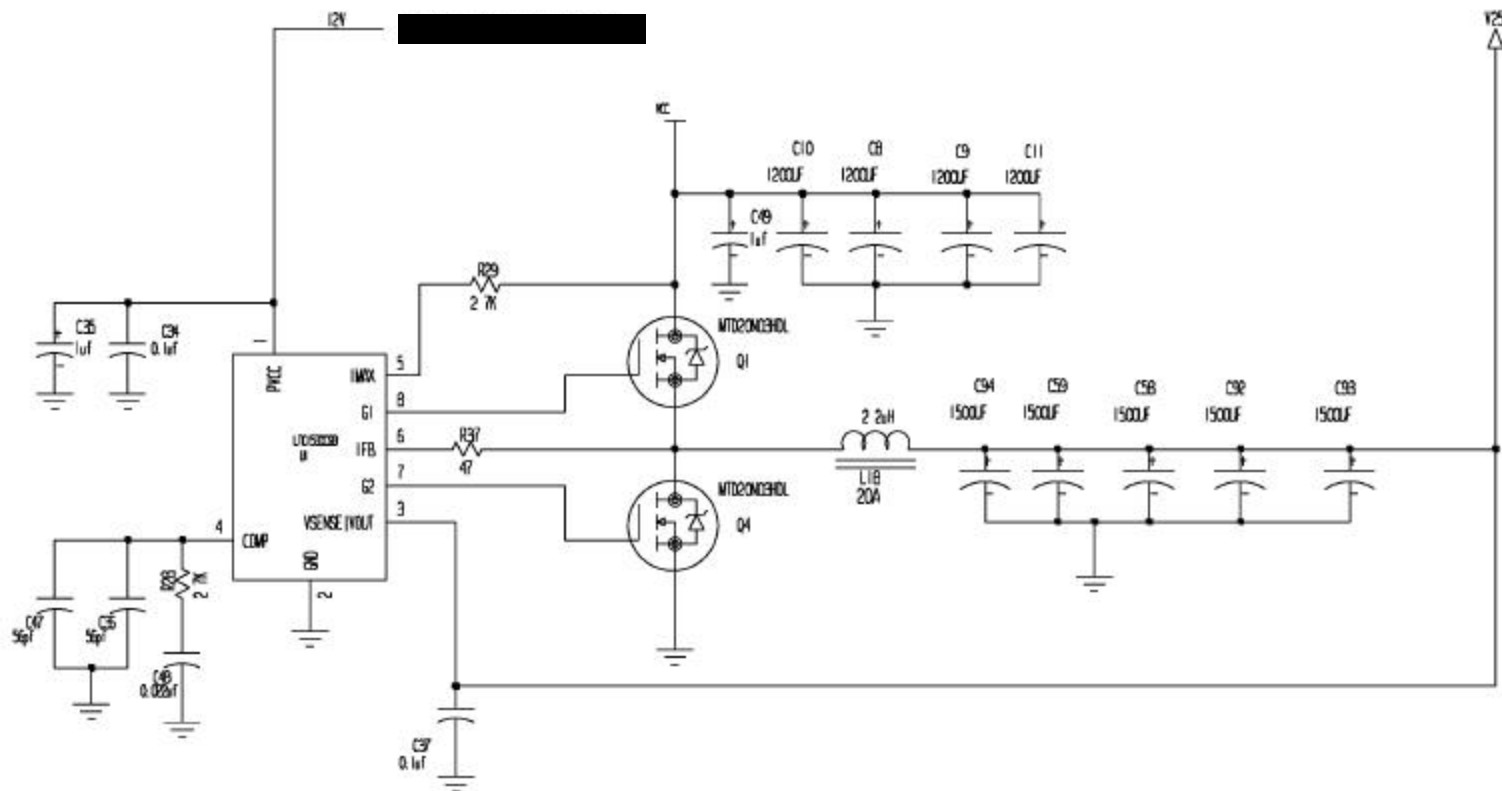- 2.5 volt regulation circuit using Linear Technology LTC1530-2.5


 
# 2.5 Volt Regulation Layout

- Regulated V2.5 ties to solid power plane under DIMM's and DRAM controller portion of Samurai DDR






# Voltage Margining


 
# VREF/VTT Margining


- Use the VREF In pin on the ML6554 to margin VREF and VTT
  - VTT and VREF out follow VREF In
- VREF specification is  $0.49 \cdot V_{DD}$  to  $0.51 \cdot V_{DD}$
- VTT specification is  $V_{REF} \pm 40\text{mV}$
- Use simple resistor divider below connected to VREF In pin on ML6554



# VDD Margining

- VDD specification is 2.3 to 2.7 volts
- To margin VDD change LTC1530-2.5 to LTC1530-ADJ
- Adjust VDD with resistor divider R1/R2.


# VDD Margining

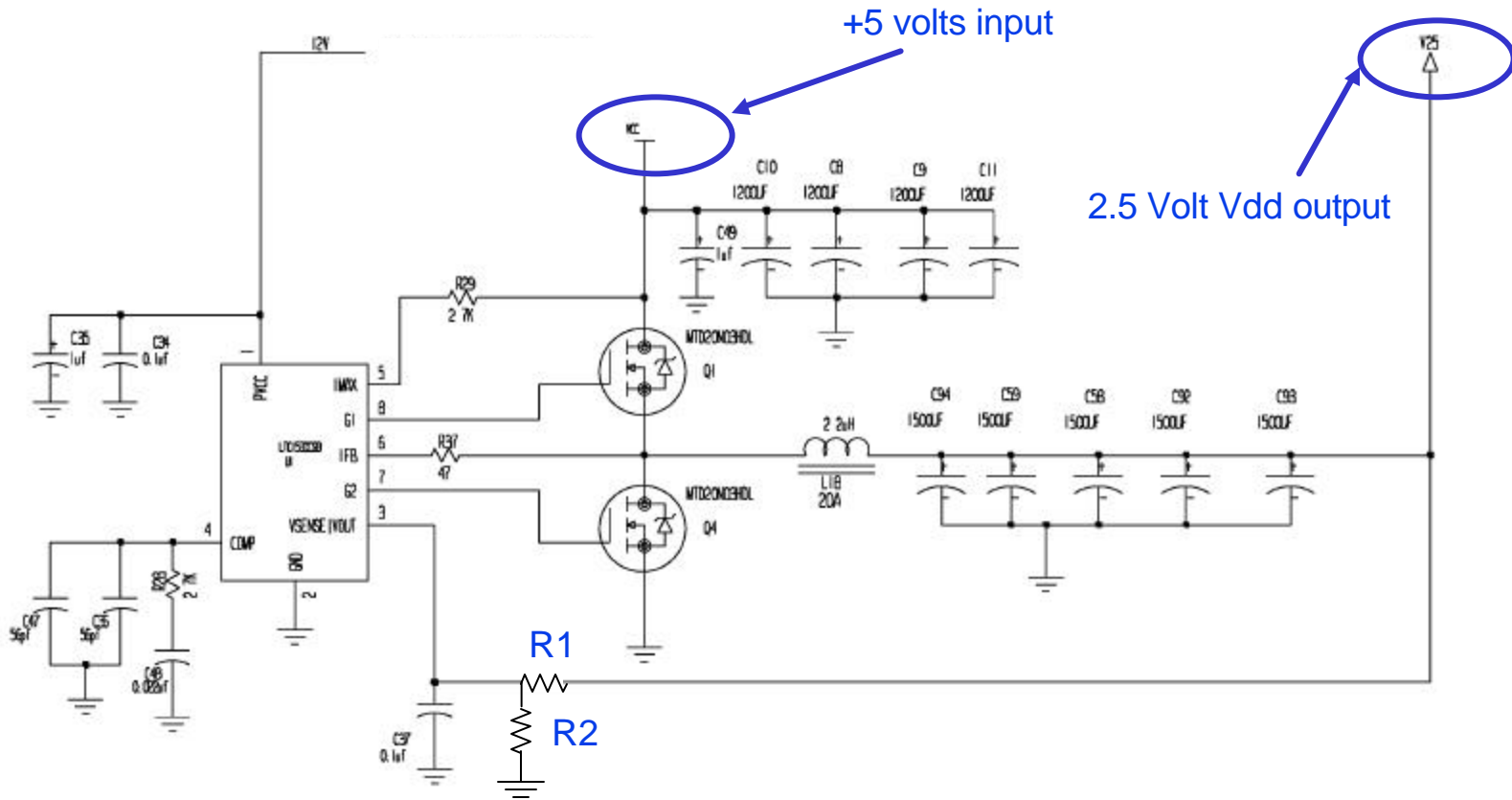


# Board Implementation



# Registered-Only Motherboard Topology

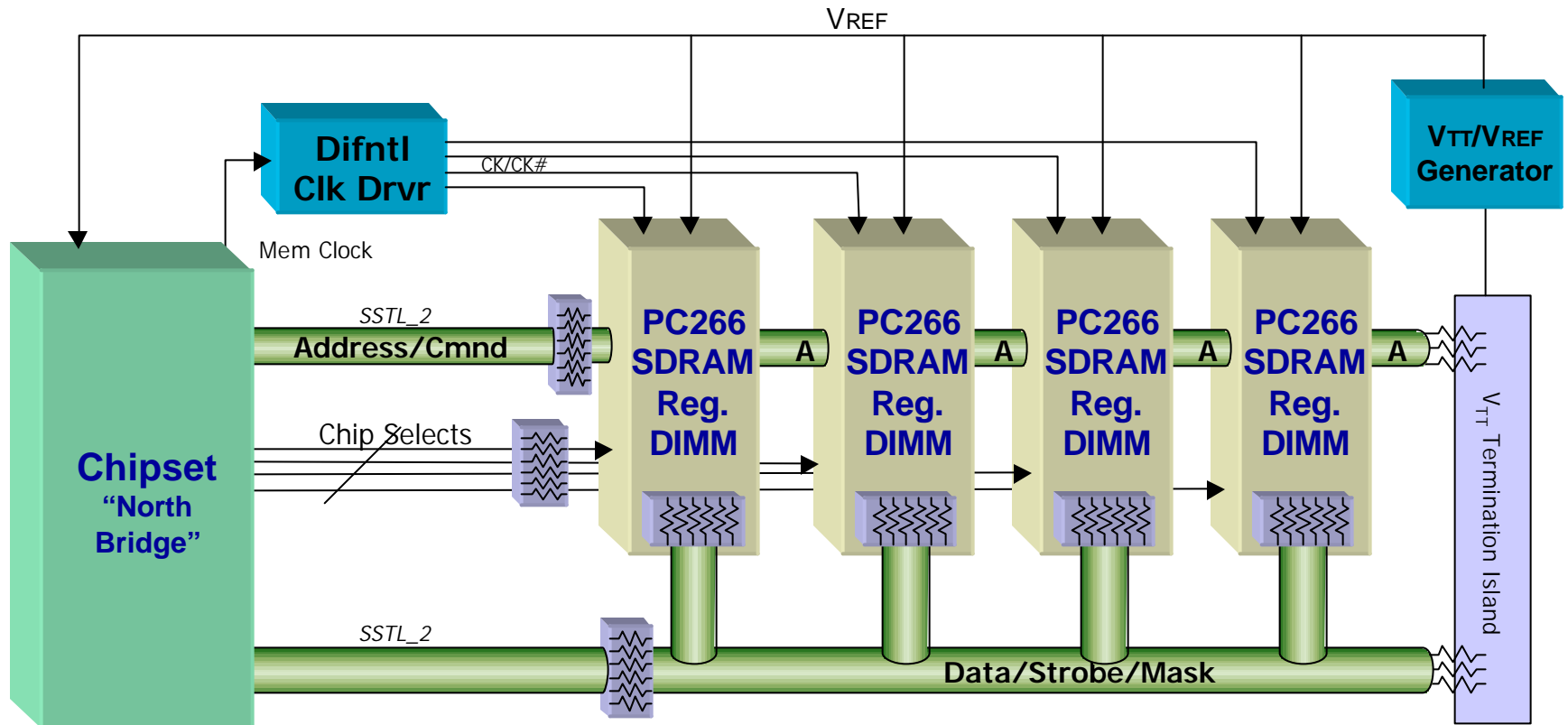
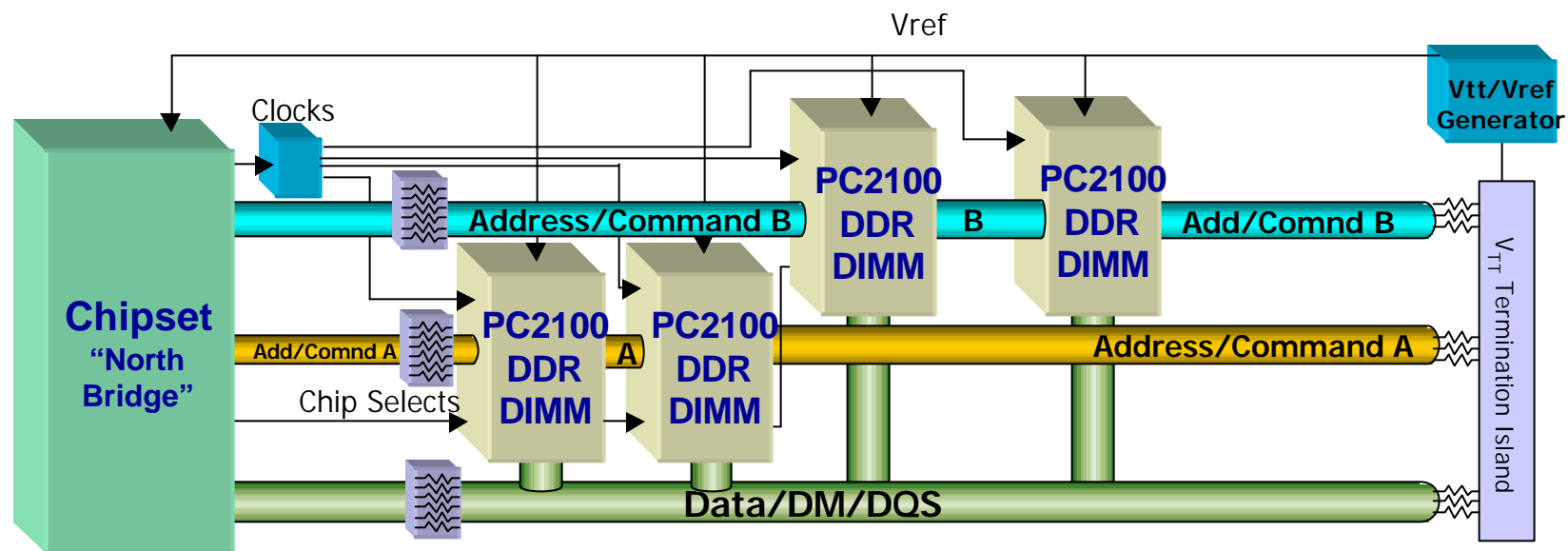
# Unbuffered/Registered Motherboard Topology



# PCB Considerations

- **PC2100 DDR can be implemented in a low-cost PCB (standard PC100 motherboard technology)**
- **Standard pad, anti-pad and via sizes can be used**
- **No additional PCB test requirements relative to PC100**





# PCB Routing

- **DDR channel can be implemented in a 2S 2P board**
  - **Controller BGA ballout determines whether a four-layer board can be used, not the memory channel**
  - **Two signal layers to get from controller to series resistor**
  - **The channel can be routed on one signal layer from the series termination resistor out, with the exception of point-to-point signals**



# Reference Motherboard Routing

- **Maintain signal reference through DDR channel**
  - Route signals on layers adjacent to a common reference plane.
  - Route each data group (8 x DQ + DQS + DM) on same layer to match propagation delays and minimize skew.
  - Address and control matching is less critical.
  - Separate data and control nets to minimize crosstalk.
- **Routing Rules**
  - 5 mil trace/15 mil space on all in group SSTL nets
  - Connector rules: 5 mil trace, 2 mil space from antipad, 7 mils from trace




# Micron Samurai DDR

## Trace length matching rules

- Match trace lengths for each data group (8 x DQ + DQS + DM) to 0.1 inch from controller to first DIMM.
- Match trace lengths to +/- 500 mils across the entire channel.
- Match composite length from controller bond pad to first DIMM pad
  - $L_{BGA} + L_{\text{controller-R}} + L_{\text{R-DIMM}} = \text{matched}$
- Length matching from last DIMM pad to parallel termination resistor is less critical


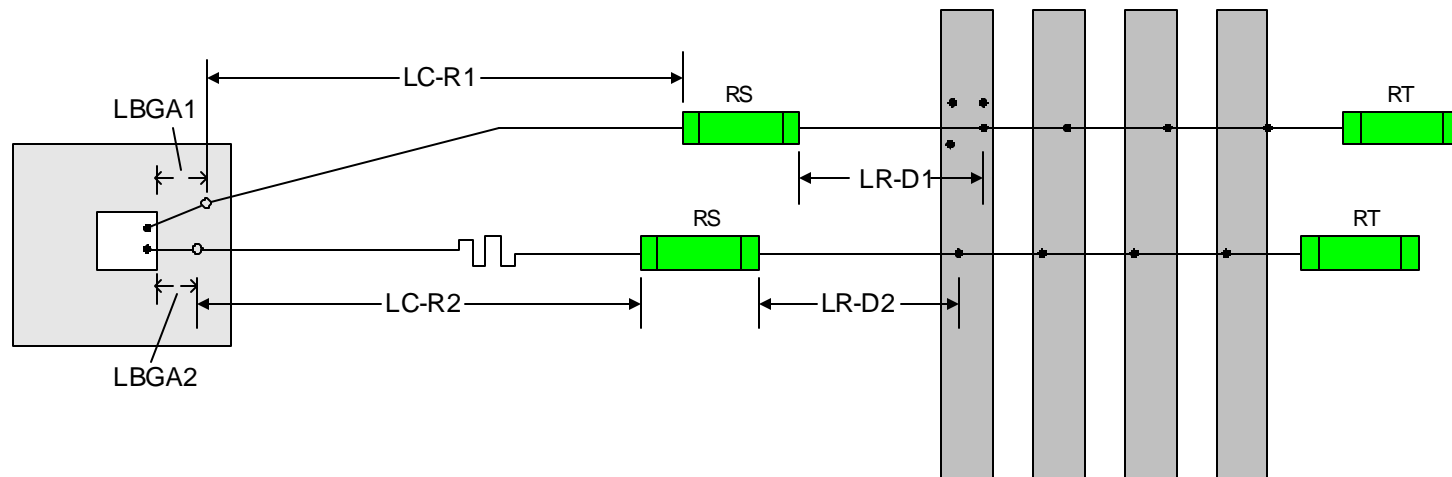
# Length Matching from Controller to 1st DIMM Pin




$$L_{BGA1} + L_{C-R1} + L_{R-D1} = L_{BGA2} + L_{C-R2} + L_{R-D2}$$

# PCB Channel Routing Through the DIMMs

- A 5-mil width / 7-mil space board will yield:
  - Three vertical signal-routing channels
  - Two diagonal signal-routing channels
  - Second layer void except for point-to-point signals
  - Lowest skew due to propagation-velocity mismatch between different signal layers



# Routing Through DIMMs

 

# Termination Resistor Placement

- **Motherboard series resistors should be close to the first DIMM**
  - **Best performance for READ from last module**
    - **Limiting case**
  - **Simplifies routing and controller congestion**




# System Design Examples






# DDR Memory Route 1st Layer

 

# DDR Memory Route


## 2nd Layer

 

# Reference Motherboard Stack-Up

## ○ Reference board stack-up

- 6 Layer Board

 

# Questions and Answers

